

Macau University of Science and Technology
CE102
Analog Circuit

Proportional, Summing Operational Circuits Report

Mao Zunjie Wang Haocheng
18098531-I011-0019 18098537-I011-0112
D1



28-11-2020

Objective

To learn how to construct different proportional, summing circuits using a op-amp.

To learn the methods to test and analyze those circuits

Device Required

Digital Multi-Meter (DMM)

Resistors

Operational Amplifier LM741

SS1798 DC Supply

Breadboard

Prelab Questions

Analyze the five circuits which are shown below, find the transfer functions of each circuit.


Calculate all the theoretical values in Table 4.2,4.3,4.4,4.5

Voltage Follower


the circuit has negative feedback, so it has virtual short, meanwhile, has virtual open

$$V_i = V_0$$

$$A_v = \frac{V_0}{V_i} = 1$$

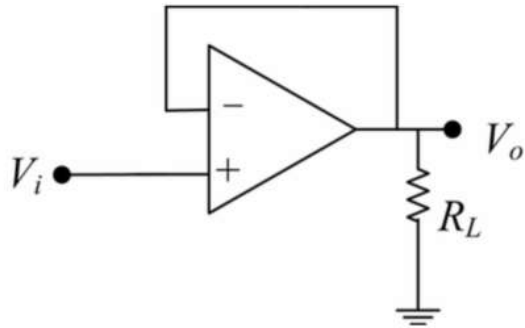

Inverting Proportional Amplifier

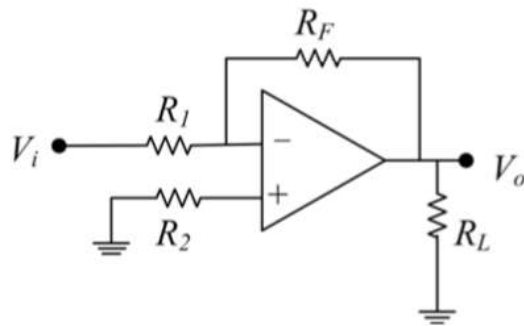

$$\frac{V_i - 0}{R_1} = \frac{0 - V_0}{R_F}$$

$$V_0 = -\frac{R_F}{R_1} V_i = -10V_i$$

$$A_v = \frac{V_0}{V_i} = -\frac{R_F}{R_1}$$


Non-inverting Proportional Amplifier

$$\frac{0 - V_i}{R_1} = \frac{V_i - V_0}{R_F}$$

$$V_i(R_1 + R_F) = V_0 R_1$$

$$V_0 = \frac{R_1 + R_F}{R_1} V_i = 11V_i$$

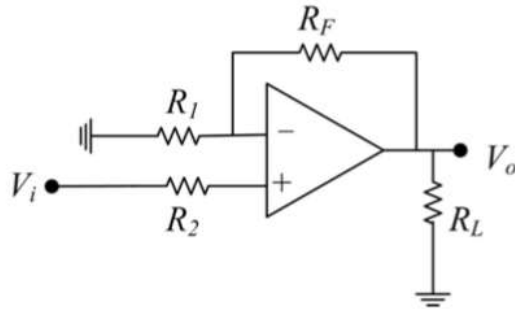
$$A_v = \frac{V_o}{V_i} = \frac{R_1 + R_F}{R_1}$$



Inverting Summing Amplifier

$$\frac{V_{i1} - 0}{R_1} + \frac{V_{i2} - 0}{R_2} = \frac{-V_o}{R_F}$$
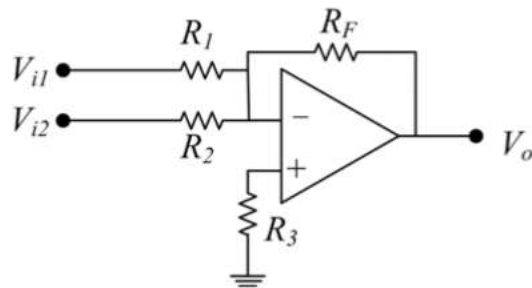
$$V_o = -\frac{(V_{i1}R_2 + V_{i2}R_1)R_F}{R_1R_2}$$




Double-Input Summing Amplifier

$$V_o = \left(1 + \frac{R_F}{R_1}\right) \left(\frac{\frac{R_3}{R_2}}{1 + \frac{R_3}{R_2}}\right) v_{I2} - \left(\frac{R_F}{R_1}\right) v_{I1}$$

$$\frac{R_3}{R_2} = \frac{R_F}{R_1}$$

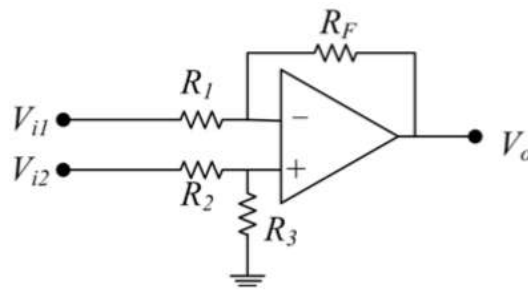
$$V_0 = \frac{R_F}{R_1} (V_{I2} - V_{I1})$$



Procedures

Circuit Set up

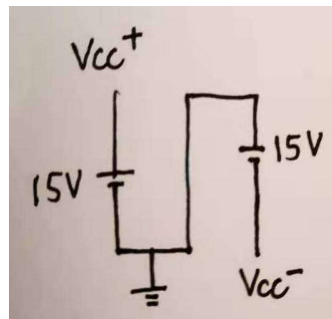Without applying the DC power, we connect the circuit on the breadboard. Carefully check all connection to make sure there is no short-circuit in whole circuit. As much as possible, make sure that the devices are not too tightly connected, and as much as possible let LM741 performed at the middle position on breadboard. Pay attention to connect Vcc power correctly.



Voltage Follower

1. Connect the Voltage follower circuit, connect the power supplies $V_{cc-} = -15V$ and $V_{cc+} = +15V$ to LM741.
2. Set $R_L = \infty$. Adjust input voltage V_i , measure input and output voltages using the DMM and fill Table 4.1.

$V_i (V)$	-2	-0.5	0	0.5	1
Actual V_i	-1.996	-0.4952	0.00165	0.4956	0.992
$V_o (V)$	-1.996	-0.496	-0.0012	0.4923	0.9889
Theory V_o	-2	-0.5	0	0.5	1

the theory calculation has been done on table,

$$V_i = V_o$$

Inverting Proportional Amplifier

1. Connect the circuit, Set $R_1 = R_2 = 10k\Omega$, $R_F = 100k\Omega$, $R_L = \infty$. Adjust the input voltage V_i and fill Table 4.2

the experimental record data are in below.

the theory calculation has been done on prelab questions,

$$V_o = -\frac{R_F}{R_1} V_i = -10V_i$$

Theory V_i (v)	0.03	0.1	0.3	1	3
Actual V_i (v)	0.0316	0.099	0.296	0.9917	2.995
Theory V_o (v)	-0.3	-1	-3	-10	-30
Actual V_o (v)	-0.339	-1.0579	-3.094	-9.40	-14.385
Error	11.5%	5.47%	3.04%	6.38%	108.55%

Also noticed, when $V_i=3V$, theory V_o is -30V, however, actual data reaches -14V nearly, the reason is that we set V_{cc} range is 15V so the actual data has already reached the saturate state.

We also calculate the relative error by subtracting the theoretical value from the measured value and dividing by the theoretical value.

Non-inverting Proportional Amplifier

1. Connect the circuit, Set $R_1 = R_2 = 10k\Omega$, $R_F = 100k\Omega$, $R_L = \infty$. Adjust the input voltage V_i and fill Table 4.3

the experimental record data are in below.

Theory V_i (v)	0.03	0.1	0.3	1
Actual V_i (v)	0.03024	0.09939	0.2959	0.9910
Theory V_o (v)	0.33	1.1	3.3	11
Actual V_o (v)	0.3012	1.1042	3.33	11.264
Error V_o (%)	9.56%	0.38%	0.9%	2.34%

the theory calculation is $V_o = \frac{R_1 + R_F}{R_1} V_i = 11V_i$

Inverting Summing Amplifier

1. Connect the circuit, Set $R_1 = R_2 = 10\text{k}\Omega$, $R_3 = R_F = 100\text{k}\Omega$, $R_L = \infty$. Adjust the input voltage V_i and fill Table 4.4

the experimental record data are in below.

the theory calculation is $V_0 = -\frac{(V_{i1}R_2 + V_{i2}R_1)R_F}{R_1R_2}$

$V_{i2} (V)$	0.3	-0.3
$V_{i1} (V)$	0.2	-0.2
Actual $V_{i2} (V)$	0.294	-0.294
Actual $V_{i1} (V)$	0.195	-0.196
Theory V_0	-5	5
Actual V_0	-5.184	5.11

Double-Input Summing Amplifier

1. Connect the circuit, Set $R_1 = R_2 = 10\text{k}\Omega$, $R_3 = R_F = 100\text{k}\Omega$, $R_L = \infty$. Adjust the input voltage V_i and fill Table 4.5

the experimental record data are in below.

the theory calculation is $V_0 = \frac{R_F}{R_1}(V_{I2} - V_{I1})$

$V_{i2} (V)$	1	2	0.2
$V_{i1} (V)$	0.5	1.8	-0.2
Actual V_{i2}	1.001	1.779	0.19
Actual V_{i1}	0.497	1.97	-0.196
Theory V_0	5	2	4
Actual V_0	5.175	2.123	4.125

Error Analysis

With respect to sources of error, real op amps cannot be ideal, for example, there is a bias current, so it is not completely virtual open, there is an offset voltage, so it is not completely virtual short, there may also be an input impedance that is not infinite and an op amp gain that is not infinite, and so on.

problems during experiment

After this experiment, we mainly started by building 5 different circuits, which further reinforced what we had learned in class, but also revealed that there were still some detail problem in our experimentation process. When we record the data, we must not forget to write down the units of the data clearly to avoid making mistakes when writing the lab report. At first we miss the voltage unit " mV " when we record the data.

summary

During the experiment, we built five different circuits on a breadboard. the volatge follower circuit do not need resistor, so it is the The Simplest Experiment, we just constuct them with wires and measured. the later four experiments need resistors we used the DMM to measure the actual input and output voltages, but also found that there were some deviations between the theoretical values and the measured actual values. After the comparison, we concluded that there may be incomplete virtual short and incomplete virtual open, which may lead to the experimental error, and also summarized some of our own shortcomings in the experiment, such as the missing units when recording the experimental data.