

Macau University of Science and Technology  
CE102  
Analog Circuit

# Emitter Follower Report

Mao Zunjie Wang Haocheng  
18098531-I011-0019 18098537-I011-0112  
D1



15-11-2020

# Objective

To understand and verify the features of an Emitter Follower circuit

To learn the methods to measure the parameters of an amplifier

# Device Required

Digital Multi-Meter (DMM)

Resistors (1k, 2k, 4.3k, 56k)

Capacitors  $10\mu \times 2$

NPN BJT 2N3904


SS1798 DC Power Supply

Breadboard

EE1651 Function Generator

Tektronix TDS210 Digital Oscilloscope

# Circuit Explanation

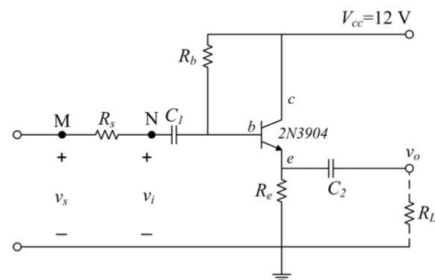

The common collector BJT amplifier, also called Emitter Follower, is one of the three basic BJT amplifier configurations. The name originates from its nearly unity voltage gain. The experimental circuit used in the lab is shown below. The parameters of the circuit are:  $R_s = 4.3\text{K}\Omega$ ,  $R_b = 56\text{K}\Omega$ ,  $R_e = 1.0\text{K}\Omega$ ,  $C_1 = C_2 = 10\mu\text{F}$ . The BJT used is 2N3904, a general purpose NPN BJT, whose datasheet can be found from <http://www.fairchildsemi.com/ds/2N/2N3904.pdf>.


## Prelab Questions

1. Find  $\beta$  of the BJT 2N3904 from its datasheet.

for  $\beta$  we recognized is called DC current gain  $h_{FE}$ , and we found some data of  $\beta$  on the datasheet.

ON CHARACTERISTICS				
DC Current Gain (Note 2) ( $I_C = 0.1\text{ mA dc}$ , $V_{CE} = 1.0\text{ V dc}$ )	2N3903	$h_{FE}$	20	-
	2N3904		40	-
( $I_C = 1.0\text{ mA dc}$ , $V_{CE} = 1.0\text{ V dc}$ )	2N3903		35	-
	2N3904		70	-
( $I_C = 10\text{ mA dc}$ , $V_{CE} = 1.0\text{ V dc}$ )	2N3903		50	150
	2N3904		100	300
( $I_C = 50\text{ mA dc}$ , $V_{CE} = 1.0\text{ V dc}$ )	2N3903		30	-
	2N3904		60	-
( $I_C = 100\text{ mA dc}$ , $V_{CE} = 1.0\text{ V dc}$ )	2N3903		15	-
	2N3904		30	-

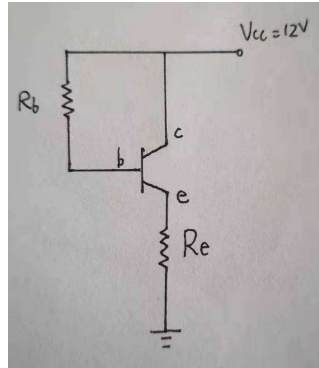2. Do DC analysis of the circuit and find Q point.



we assume  $\beta$  is 100, write KVL from  $V_{cc}$  to ground

$$V_{cc} - i_b R_b - 0.7 - (1 + \beta) i_b R_e = 0$$

Solve  $i_b = 0.072 \text{ mA}$


$$I_e = \beta i_b = 7.2 \text{ mA}$$

$i_c = \beta i_b = 7.2 \text{ mA}$ , so we take  $\beta = 100$

$$V_{cc} - V_{CEQ} - (1 + \beta) i_b R_e = 0$$

$$V_{CEQ} = 9.728 \text{ V}$$

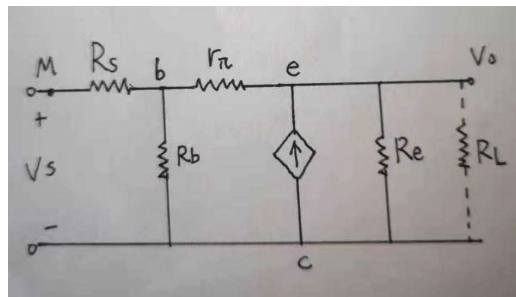3. Do ac analysis of the circuit and find  $A_v$ ,  $R_i$ ,  $R_o$ .



$$V_o = (1 + \beta) i_b R_e$$

$$V_0=7.272\text{V}$$

$$V_i=i_b r_\pi+i_e R_e=7.226\text{V}$$

$$V_s = \left( \frac{i_b r_\pi + (1+\beta)i_b R_e}{R_b} + i_b \right) R_s + i_b r_\pi + (1 + \beta)i_b R_e$$

$$V_s=8.167\text{V}$$

$$A_v=\frac{V_0}{V_s}=0.89$$

$$R_i=\left(\frac{V_i}{\left(\frac{i_b r_\pi + (1+\beta)i_b R_e}{R_b} + i_b\right)}\right)=35.95\text{k}\Omega$$

$$R_0=R_e=1\text{k}\Omega$$

## Procedures

### Circuit Set up

Without applying the dc power, connect the circuit on the breadboard. Carefully check all connection to make sure there is no short-circuit in your setup. As much as possible, make sure that the devices are not too tightly connected

When getting BJT CN3904, note that the cut side of the cylinder faces you, 'ebc' from left to right.

### Measurement of DC operational point

Turn on the +12V DC supply, Note that when you see a value, press the onoff button and then continue. Use the functional generator to generate a 1kHz, 2 V (peak-to-peak) sinusoidal signal and apply it to point M. Using the two channels of the oscilloscope to monitor  $V_i$  and  $V_0$ . Check if the output voltage  $V_0$  is correct. Then remove the ac input signal from point M. Using the DMM to measure the dc voltages of the three terminals of the BJT and fill Table. Those values show where the location of Q-point is.

the experimental record data are in below.

At Prelab part, my theory caculation is  $I_e$  is 7.2 mA, and real tested data as shown is

Table 2.1: DC operational point

$R_e$ (k $\Omega$ )	$V_B$ (V)	$V_C$ (V)	$V_E$ (V)	$V_{CE}$ (V)	$I_E = \frac{V_E}{R_e}$ (mA)
1	9.604	8.930	3.059	3.059	8.93

8.93 mA, it has a little error. Introduces some errors into the overall experiment, possibly due to errors in the bias voltage, as well as errors in the accuracy of the measurement instrument itself. Taken together, this may be a signal resistance and op amp bias problem, or an op amp supply voltage problem, or an op amp input/output range, or an output driving capability problem.

## Measurement of Amplifier Voltage Gain

Connect a 1 k $\Omega$  resistor as the load RL and apply a 1 kHz ac signal to point M. Using the two channels of the oscilloscope to monitor  $V_i$  and  $V_o$ . Adjust the amplitude of input signal at different values and check the amplitude of output  $V_o$ .

the experimental record data are in below.

Table 2.2: Voltage Gain of a BJT Amplifier

$v_{i,peak-to-peak}$ (V)	$v_{o,peak-to-peak}$ (V)	$A_v = \frac{v_o}{v_i}$
1 V	2	2
1.6 V	3	1.875
2.4 V	4.48	1.866
3 V	5.52	1.84

and my theory caculation is

$$V_0 = (1 + \beta) i_b R_e$$

$$V_0 = 7.226 \text{ V}$$

$$V_i = i_b r_\pi + i_e (R_e \parallel R_L) = 3.613 \text{ V}$$

$$\frac{V_0}{V_i} = 2$$

Introduces some errors into the overall experiment, possibly due to errors in the bias voltage, as well as errors in the accuracy of the measurement instrument itself

## Measurement of Input Resistance

Apply a 1 kHz, 1 V (peak-to-peak) ac signal to point M. Using the two channels of the oscilloscope to monitor  $V_i$  and  $V_0$  and make sure the output is not distorted. Using the DMM in ac voltage mode to measure the potential of point M and N (i.e. the rms voltages of  $V_s$  and  $V_i$ ). Please also measure the actual value of  $R_s$  and fill in the table. The input resistance can be calculated with the equation in Table 2.3.

the experimental record data are in below.

as shown before, theory calcualation is 
$$R_i = \frac{V_i}{\left( \frac{i_b r_\pi + (1 + \beta) i_b R_e}{R_b} + i_b \right)} = 35.95 \text{ k}\Omega$$

Table 2.3: Measurement of Input Resistance

$R_s$ (k $\Omega$ )	$v_s$ (V)	$v_i$ (V)	$R_i = R_s / (\frac{v_s}{v_i} - 1)$ (k $\Omega$ )
4.3	0.685	0.626	47.77

Introduces some errors into the overall experiment, possibly due to errors in the bias voltage, as well as errors in the accuracy of the measurement instrument itself.

## Measurement of Output Resistance

Apply a 1 kHz AC signal to point M. Using Channel 1 of the oscilloscope to monitor  $V_i$  at point N. Adjust the Function Generator to get  $V_{i,\text{peak}}$  to peak = 2V . Without load, using Channel 2 to measure no-load output voltage  $V_{0,\text{rms}}$ ; with  $R_L = 2 \text{ k}\Omega$ , using Channel 2 to measure load output voltage  $V_{L,\text{rms}}$ . Please also measure the actual value of  $R_L$  and fill in the table. The input resistance can be calculated with the equation in Table 2.4

the experimental record data are in below.

Table 2.4: Measurement of Output Resistance

$R_L \text{ (k}\Omega\text{)}$	$v_{o,\text{rms}}$ (V) at no-load	$v_{L,\text{rms}}$ (V) at $R_L = 2 \text{ k}\Omega$	$R_o = (\frac{v_{o,\text{rms}}}{v_{L,\text{rms}}} - 1)R_L \text{ (k}\Omega\text{)}$
2.0	1.296	1.281	0.0234

## Observation of the Maximum Swing

Apply a 1 kHz ac signal to point M. Using the two channels of the oscilloscope to monitor  $v_i$  and  $v_o$ . Adjust the Function Generator to increase the amplitude of input ac signal  $v_i$  until the output voltage  $v_o$  is distorted.

After the experiment, the maximum input amplitude is 3.52V nearly

## summary

For the same measurement point on the circuit, or any other measurement, the measured value and the theoretical value will produce a deviation, this deviation is related to the accuracy of the measurement equipment, that is, there is an inherent error. In the circuit, the deviation of the output signal from the theoretical value to the measured value is mainly determined by the non-linear characteristics of the transistor and the frequency response capability.